

4:1 MUX

Code for MUX Module:


```
-----  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;  
  
-- Uncomment the following library declaration if instantiating  
-- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity mux is  
    Port ( D : in  STD_LOGIC_VECTOR (3 downto 0);  
          Y : out  STD_LOGIC;  
          S : in  STD_LOGIC_VECTOR (1 downto 0));  
end mux;  
  
architecture mux_arch of mux is  
  
begin  
    -- S, D are passed inside the sensitivity list  
    process (S, D)  
    begin  
        if (S="00") then  
            Y<= D(0);
```

```
    elsif(S="01") then
        Y<=D(1);
    elsif(S="10") then
        Y<=D(2);
    else
        Y<=D(3);
    end if;

end process;

end mux_arch;
```

RTL Schematic:

 

Time Bench:

stim_proc: process

begin

-- hold reset state for 100 ns.

wait for 100 ns;

D<="1010";

S<="00";

wait for 100 ns;

S<="01";

wait for 100 ns;

S<="10";

wait for 100 ns;

S<="11";


-- wait for <clock>_period*10;

-- insert stimulus here

wait;

end process;

TIMING DIAGRAM:

 

2:4 Line Decoder Using Case:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity two_four_decoder is
    Port ( D : in  STD_LOGIC_VECTOR (1 downto 0);
          Y : out  STD_LOGIC_VECTOR (3 downto 0));
end two_four_decoder;

architecture decoder_arch of two_four_decoder is

begin

process (D)
begin


case D is
when "00"=>
    Y<="0001";
when "01"=>
```

```

        Y<="0010";
when "10=>
        Y<="0100";
when others=>
        Y<="1000";
end case;
end process;

end decoder_arch;

```

 

Code for Decoder Test Bench

```

stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    D<="00";

```

```


        wait for 100 ns;
        D<="01";
        wait for 100 ns;
        D<="10";
        wait for 100 ns;
        D<="11";

--      wait for <clock>_period*10;

-- insert stimulus here

    wait;
end process;

```

 

4-bit Magnitude Comparator

Code for 4-bit magnitude comparator

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity comparator is
    Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
          B : in  STD_LOGIC_VECTOR (3 downto 0);
          L : out  STD_LOGIC;
          E : out  STD_LOGIC;
          G : out  STD_LOGIC);
end comparator;

architecture comparator_arch of comparator is

begin
```


```
process (A, B)
begin

    if(A>B) then
        G<='1';
        L<='0';
        E<='0';

    elsif(A<B) then
        G<='0';
        L<='1';
        E<='0';

    else
        G<='0';
        L<='0';
        E<='1';

    end comparator_arch;
```

 Code for Test Bench 4-bit Comparator:

```
stim_proc: process
  begin
    -- hold reset state for 100 ns.

    A<="0010";
    B<="0100";

    wait for 100 ns;
    A<="1000";
    B<="0101";

    wait for 100 ns;
```

```
A<="1011";
```

```
B<="1011";
```


```
--      wait for <clock>_period*10;
```

```
-- insert stimulus here
```

```
wait;
```

```
end process;
```

TIMING Diagram:

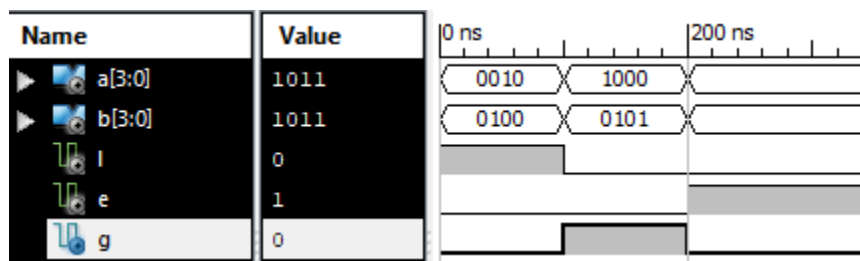

JK Flip-Flop:

Code for JK VHDL module:

```
library IEEE;
```

```

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity JK_FF is
    Port ( J : in  STD_LOGIC;
          K : in  STD_LOGIC;
          CLK : in  STD_LOGIC;
          RST : in  STD_LOGIC;
          Q : out  STD_LOGIC;
          Qbar : out  STD_LOGIC);
end JK_FF;

architecture JK_FF_arch of JK_FF is
    signal temp: STD_LOGIC := '0';
begin

    process(RST, CLK, J, K)
    begin
        if(RST='0') then
            temp<='0';
--clk' event is for triggering event clock?
            elsif (CLK='1' and CLK' Event) then

```

```

        if(J='0' and K='0') then
            temp<=temp;
        elsif(J='0' and K='1') then
            temp<='0';
        elsif(J='1' and K='1') then
            temp<='1';
        else
            temp<= not temp;
        end if;

    end if;


Q<=temp;
Qbar<=not temp;

end process;

end JK_FF_arch;

```

RTL Schematic:

 

JK Flip Flop Test Bench Code:

```
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    RST<='0';
    CLK<='1';
    J<='1';
    K<='0';

    wait for 100 ns;

    RST<='1';
```

```
CLK<='1';
```

```
J<='0';
```

```
K<='0';
```

```
wait for 100 ns;
```

```
J<='0';
```

```
K<='1';
```

```
wait for 100 ns;
```

```
J<='1';
```

```
K<='0';
```

```
wait for 100 ns;
```


```
J<='1';
```

```
K<='1';
```

```
-- insert stimulus here
```

```
wait;
```

```
end process;
```

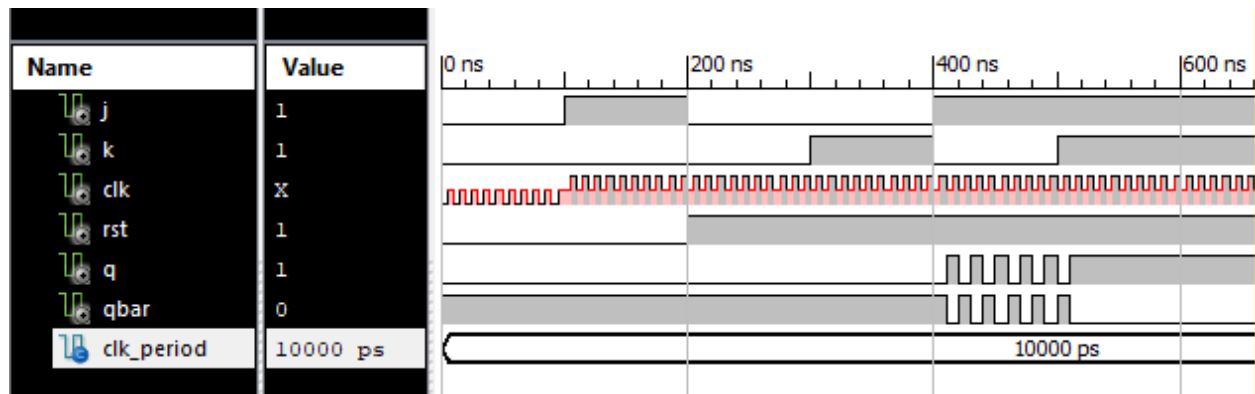

4 bit counter:

Code for Counter VHDL Module:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
```

```

-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity four_counter is
    Port ( CLK : in  STD_LOGIC;
           RST : in  STD_LOGIC;
           Count : out  STD_LOGIC_VECTOR (3 downto 0));
end four_counter;

architecture four_counter_arch of four_counter is
    signal tcount: std_logic_vector(3 downto 0):="0000";
begin

    process(CLK, RST)
    begin


        if(RST='0') then
            tcount<="0000";
        elsif (CLK='1' and CLK' Event) then
            tcount<=tcount+1;

        end if;
        Count<=tcount;
    end process;


end four_counter_arch;

```


RTL Schematic:

 

Or

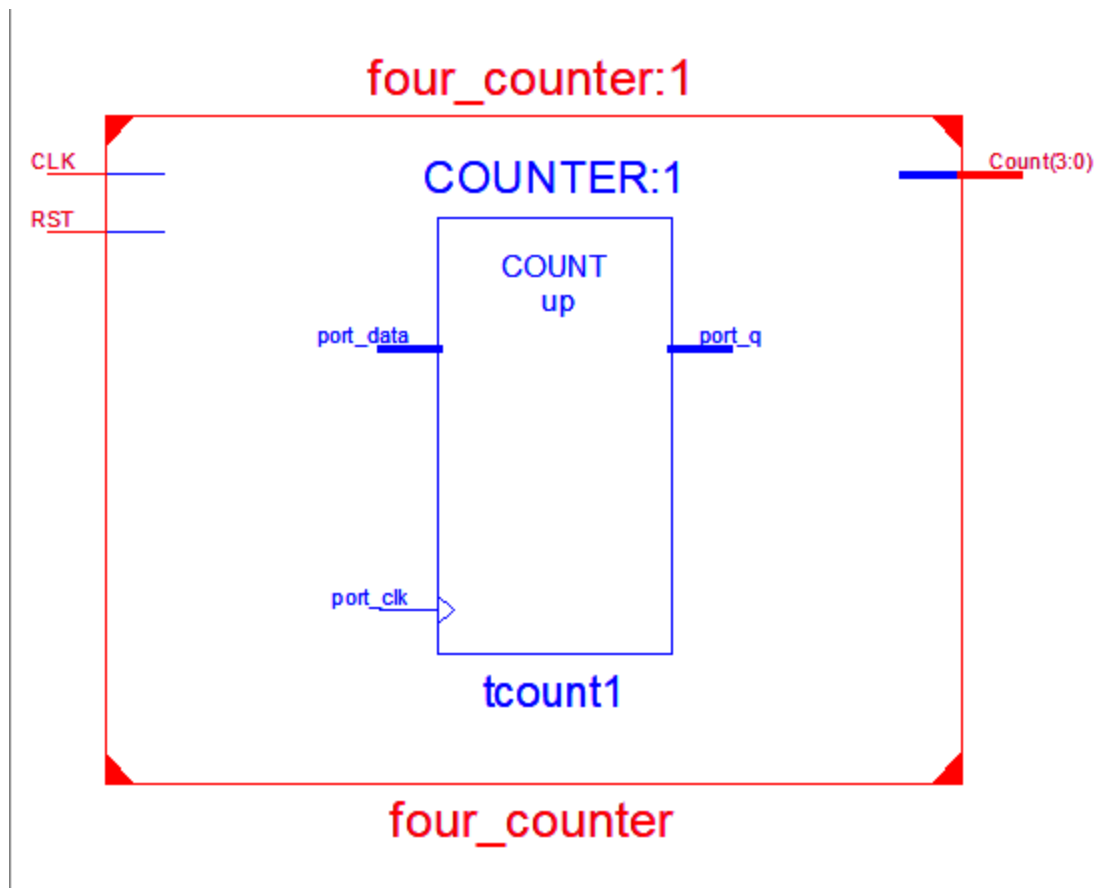

Code for 4-bit Counter Test Bench

```
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
```

```

RST<='0';

    CLK<='1';

    wait for 100 ns;

    RST<='1';
    CLK<='1';
    -- insert stimulus here

    wait;
end process;

```

Timing Diagram:

